

Grade-09

Weekly planner

Week-110

Subject: Physics (0625)

Name of the faculty: S.M Tanvir

| Day: Sunday | Learning objectives and Outcomes: | | |
|-------------|---|----------------------|---------|
| and Tuesday | Students will be able to understand and | | |
| Date: | calculate the current in series and narallel | Tools and | Special |
| 19/03/24 to | circuits. | resources | remarks |
| 21/03/24 | | | |
| 19/03/24 | Ice-Breaking Session (5 minutes): | Text Book | |
| Day-02 | Question 1 : "Imagine you have a string of holiday lights. | Marker | |
| | If one build goes out, what happens to the rest of the | Board Video clins | |
| | ngnis: Discuss with your partner. | Worksheets | |
| | connected to a single power strip? How do you think | Worksheets | |
| | the electricity flows through them? Share your | | |
| | thoughts with the class" | | |
| | Development activities- (20 minutes) | | |
| | Series Circuit: | | |
| | 1. Explain that in a series circuit, components are | | |
| | connected end-to-end, forming a single | | |
| | pathway for current flow. | | |
| | 2. Draw a simple series circuit on the board and | | |
| | label the components. | | |
| | 3. Demonstrate how to calculate total resistance | | |
| | in a series circuit (summing individual | | |
| | resistances). | | |
| | 4. Show how to calculate current using Ohm's | | |
| | Law $(I = V/R)$. Provide an example problem for | | |
| | students to solve individually or in pairs. | | |
| | Parallel Circuit: | | |
| | 1. Explain that in a parallel circuit, components | | |
| | are connected in multiple branches, allowing | | |
| | current to take different paths. | | |
| | 2. Draw a simple parallel circuit on the board and | | |
| | label the components. | | |
| | 3. Demonstrate how to calculate total resistance | | |
| | in a parallel circuit (using reciprocal formula or | | |
| | shortcut). | | |
| | 4. Show how to calculate total current in a parallel | | |
| | circuit using Ohm's Law. | | |

| | 5. Provide an example problem for students to | |
|--------|--|--|
| | solve | |
| | | |
| | Guided Practice (5 minutes): Divide students into small | |
| | groups. Provide each group with a worksheet | |
| | containing a mix of series and parallel circuit problems. | |
| | Circulate the room to provide assistance and answer | |
| | questions. | |
| | Closing activities- (5 minutes) | |
| | Review key concepts of series and parallel circuits. | |
| | Summarize the methods for finding total resistance and | |
| | current in each type of circuit. Encourage students to | |
| | ask any remaining questions. | |
| Day-02 | Ice-Breaking Session (5 minutes): | |
| | Welcome the students to the lesson and briefly review | |
| | the topic or concept covered in the previous class. | |
| | Explain the importance of practicing problem-solving | |
| | skills and the purpose of today's active lesson. | |
| | Case study: Problem exam style questions(chapter-19) | |
| | 1. Divide the class into small groups of 3-4 | |
| | students each. | |
| | 2. Provide each group with a set of exercise | |
| | questions related to the topic. | |
| | 3. Instruct the groups to work together to solve | |
| | the questions. | |
| | 4. Encourage collaboration and discussion within | |
| | the groups. | |
| | 5. Walk around the classroom, offering assistance | |
| | and guidance as needed. | |
| | Closing activities- (5 minutes) | |
| | Summarize the key points covered during the lesson. | |
| | Reinforce the importance of practicing problem-solving | |
| | skills regularly. Encourage students to continue | |
| | reviewing and solving exercise questions outside of | |
| | class to strengthen their understanding of the material. | |
| | | |

| Differentiation: By content / Process/ | Home work: Practice | Assessment tools & | |
|--|---------------------|-----------------------|--|
| Product/Environment/Class performance. | classwork. | strategies: Formative | |
| | | assessment | |
| | | Reflection (if any): | |